



LAB01 Exercise Design Review

Lecturer : KH
Date:2020/10/07


Outline

- Sort
- Normalization
- Equations
- Normalization + Equations



6 numbers sort architecture

- Use 12 comparators

 

sorter architecture(1/3)


	unsigned	signed		unsigned	signed
0000	0	0	1000	8	-8
0001	1	1	1001	9	-7
0010	2	2	1010	10	-6
0011	3	3	1011	11	-5
0100	4	4	1100	12	-4
0101	5	5	1101	13	-3
0110	6	6	1110	14	-2
0111	7	7	1111	15	-1



sorter architecture(2/3)


unsigned

In0[3]	In1[3]	
0	0	Depends on last three bits
0	1	$in0 < in1$
1	0	$in0 > in1$
1	1	Depends on last three bits

 

signed

In0[3]	In1[3]	
0	0	Depends on last three bits
0	1	$in0 > in1$
1	0	$in0 < in1$
1	1	Depends on last three bits

 

$wire\ flg = (\sim s \ \& \ (in0[3] \ | \ \sim in1[3])) \ | \ (s \ \& \ (\sim in0[3] \ | \ in1[3]))$
 $wire\ abs_big = (\sim s \ \& \ in0[3] \ \& \ \sim in1[3]) \ | \ (s \ \& \ \sim in0[3] \ \& \ in1[3])$

sorter architecture(3/3)

- Original -> use 5 bits 2's complement comparator
- Optimized -> use 3 bits unsigned comparator and 6 inv 4and 4or gates

```
module comp(  
    input      s,  
    input  [3:0] in0,  
    input  [3:0] in1,  
    output [3:0] out0,  
    output [3:0] out1  
);  
  
    wire abs_big = (~in0[3] & in1[3] & s) | (~s & in0[3] & ~in1[3]); ///  
    wire flg = ( (s & (~in0[3] | in1[3])) | (~s & (in0[3] | ~in1[3])) ); ///  
    wire bigger = (in0[2:0] > in1[2:0]) ;  
  
    assign out0 = (abs_big | (flg & bigger) ) ? in0 : in1;  
    assign out1 = (abs_big | (flg & bigger) ) ? in1 : in0;  
endmodule
```



Convert unsigned number to signed number

- Let unsigned number and signed number use same hardware resources

```
wire signed [4:0] sort_result0 = {{s&sort_tmp0[3]},sort_tmp0};  
wire signed [4:0] sort_result1 = {{s&sort_tmp1[3]},sort_tmp1};  
wire signed [4:0] sort_result2 = {{s&sort_tmp2[3]},sort_tmp2};  
wire signed [4:0] sort_result3 = {{s&sort_tmp3[3]},sort_tmp3};  
wire signed [4:0] sort_result4 = {{s&sort_tmp4[3]},sort_tmp4};  
wire signed [4:0] sort_result5 = {{s&sort_tmp5[3]},sort_tmp5};
```



Normalization

- Original -> use 6 MUX and 6 Subtractors

```
wire signed [4:0] norm_result0 = (opt[2]) ? (sort_result0 - avg) : sort_result1;  
wire signed [4:0] norm_result1 = (opt[2]) ? (sort_result1 - avg) : sort_result2;  
wire signed [4:0] norm_result2 = (opt[2]) ? (sort_result2 - avg) : sort_result3;  
wire signed [4:0] norm_result3 = (opt[2]) ? (sort_result3 - avg) : sort_result4;  
wire signed [4:0] norm_result4 = (opt[2]) ? (sort_result4 - avg) : sort_result5;  
wire signed [4:0] norm_result5 = (opt[2]) ? (sort_result5 - avg) : sort_result6;
```

- Optimized -> use 1 MUX and 6 Subtractors

```
wire signed [4:0] norm_val = (opt[2]) ? avg : 0;  
wire signed [4:0] norm_result0 = sort_result0 - norm_val;  
wire signed [4:0] norm_result1 = sort_result1 - norm_val;  
wire signed [4:0] norm_result2 = sort_result2 - norm_val;  
wire signed [4:0] norm_result3 = sort_result3 - norm_val;  
wire signed [4:0] norm_result4 = sort_result4 - norm_val;  
wire signed [4:0] norm_result5 = sort_result5 - norm_val;
```


Equations(1/2)

- Eq0 : Use 1 Subtractor , 1 Adder , 1 Multiplier and 1 Divider
- Eq1 : Use 1 Subtractor , 1 Adder , 1 Multiplier and 1 Comparator

```
//=====
//      Eq0
//=====
|   wire [8:0] eq0 = (n0-n1*n2+n5)/3;
//=====
//      Eq1
//=====
|   wire signed [8:0] eq1_tmp = (n3<<1 + n3) - n0*n4;
|   wire signed [8:0] eq1 = (eq1_tmp > 0) ? eq1_tmp : eq1_tmp * -1;
```



Equations(2/2)

- Eq0 / Eq1 share 1 Subtractor , 1 Adder , 1 Multiplier
- Cost : need 6 MUX to select input data

```
wire signed [5:0] add_in1 = (equ) ? n3*2 : n0;  
wire signed [4:0] add_in2 = (equ) ? n3 : n5;  
wire signed [4:0] mul_in1 = (equ) ? n0 : n1;  
wire signed [4:0] mul_in2 = (equ) ? n4 : n2;  
wire signed [8:0] tmp0 = (add_in1 + add_in2) - (mul_in1 * mul_in2);
```



Normalization + Equations

- In fact , we just need 4 Subtractors
- Original -> use 6 Subtractors
- Optimized -> use 4 Subtractors

1 2 3 4

1. Eq0 : $((n0 - n1 * n2 + n5) / 3)$ (round-down the answer if it is not integer)

For example, if result is -3.75, round down to -3,
if result is 5.5, round down to 5

1 2 3


2. Eq1 : $|n3 * 3 - n0 * n4|$

(Hint: Try to use behavior modeling description instead of gate level description)

Normalization + Equations architecture

```

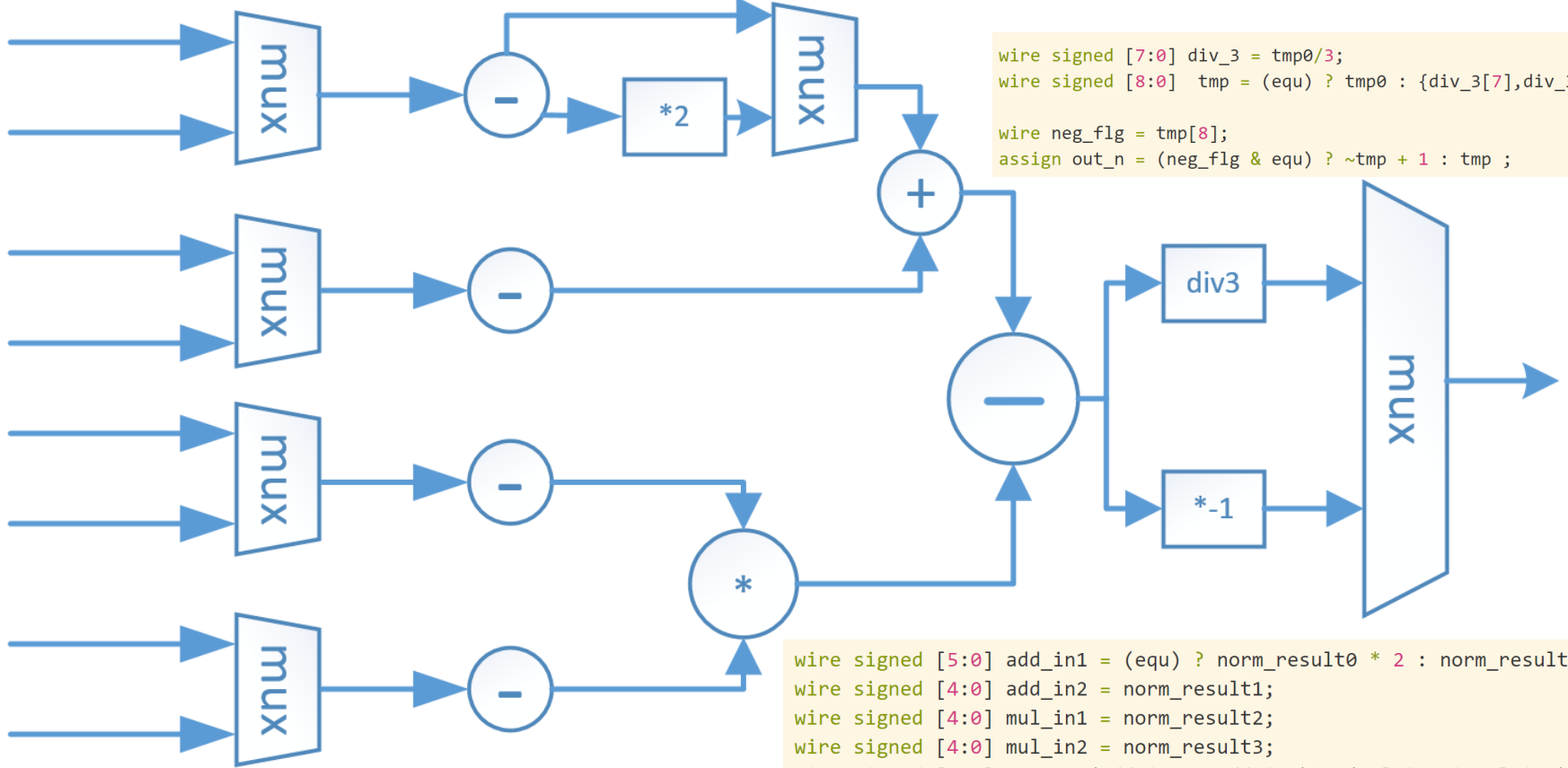wire signed [4:0] norm_mux_out0 = (equ) ? sort_result3 : sort_result0;
wire signed [4:0] norm_mux_out1 = (equ) ? sort_result3 : sort_result5;
wire signed [4:0] norm_mux_out2 = (equ) ? sort_result0 : sort_result1;
wire signed [4:0] norm_mux_out3 = (equ) ? sort_result4 : sort_result2;
    
```



```

wire signed [7:0] div_3 = tmp0/3;
wire signed [8:0] tmp = (equ) ? tmp0 : {div_3[7],div_3};

wire neg_flg = tmp[8];
assign out_n = (neg_flg & equ) ? ~tmp + 1 : tmp ;
    
```

```

wire signed [5:0] add_in1 = (equ) ? norm_result0 * 2 : norm_result0;
wire signed [4:0] add_in2 = norm_result1;
wire signed [4:0] mul_in1 = norm_result2;
wire signed [4:0] mul_in2 = norm_result3;
wire signed [8:0] tmp0 = (add_in1 + add_in2) - (mul_in1 * mul_in2);
    
```